

# Snap Circuits Jr. STEM Challenge

## Series Circuit Engineering Challenge

Group Members: \_\_\_\_\_ Date: \_\_\_\_\_



### Objective

Build a working **SERIES CIRCUIT** where both the speaker and propeller work successfully using all four components of a circuit.

### The Four Components of a Circuit

1 Power Source



2 Conductors



3 Load(s)



4 Switch



### Materials

- Snap Circuits Jr. kit
- Battery pack
- Snap wires
- Switch
- Speaker
- Motor/Propeller
- Pencil



### Challenge Instructions

#### Your Mission

Create a **SERIES CIRCUIT** where:

- The speaker produces sound
- The propeller spins
- All four components of a circuit are included





## Before You Build

### Predict:

What do you think will happen when the switch is turned on?

---

---

---

---




## Build Your Circuit

### Remember:

A series circuit has **only ONE** path for electricity to travel.

Make sure your circuit includes:

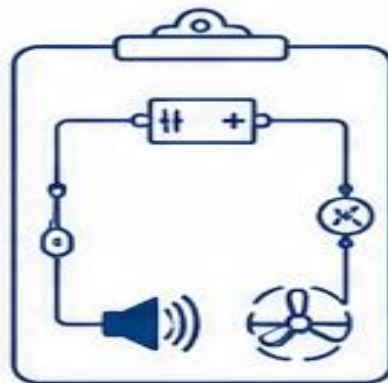- Power Source
- Conductors
- Load(s)
- Switch



## Observation Questions

1. What happened when you turned the switch ON?

---

---

---

2. What happened when you turned the switch OFF?

---

---

---

**3** Why is the battery important in the circuit?

---

---

---

---

**4** Which parts of your circuit are the loads?

---

---

---

---

**5** What would happen if one conductor was removed?

---

---

---

---



### Illustrate Your Final Circuit

Draw your final working **SERIES CIRCUIT** below.

Be sure to LABEL:

- Power Source (red)
- Conductors (blue)
- Load(s) (green)
- Switch (orange)



### Reflection

What was the hardest part of building your circuit?

---

---

---

What did you learn about electricity and circuits from this activity?

---

---

---



### Teacher Check

Circuit Complete: \_\_\_\_\_

Speaker Working: \_\_\_\_\_

Propeller Working: \_\_\_\_\_

All 4 Components Identified: \_\_\_\_\_

Student Explanation Complete: \_\_\_\_\_